



NATIONAL OPEN UNIVERSITY OF NIGERIA
University Village, 91 Cadastral Zone, Nnamdi Azikwe Expressway, Jabi, Abuja
FACULTY OF SCIENCES
COMPUTER SCIENCE DEPARTMENT
2021 EXAMINATIONS

CIT 344 – Introduction To Computer Design

Credit: 3 units

TIME ALLOWED: 2½ Hours

INSTRUCTION: Answer Question 1 and any other FOUR (4) Questions

QUESTION ONE

(22 marks)

1. (a) i. Convert 637 in decimal to binary *(1½ marks)*
ii. Convert 234 in decimal to binary *(1½ marks)*
iii. Convert 1001101 in base two to base ten *(2 marks)*
iv. Find the BCD addition of 324 and 234 *(2 marks)*

- (b) Given this expression $(a*b) + (a*c)$, then:
i. Construct the truth table *(1½ marks)*
ii. write the minterms *(½ marks)*
iii. Write the SOP *(½ marks)*
iv. Draw Karnaugh map *(½ marks)*
v. Simplify the expression *(½ marks)*
vi. Draw the logic gates for the simplified expression *(½ marks)*

(c)

- i. What is a Multiplexer? *(2 marks)*
ii. What are the areas of application of Multiplexer? *(1 mark)*
iii. What is a Ring Counter? *(2 marks)*
(d) List and explain three commercially available 4-bit ALUs *(3 marks)*
(e) Give the meaning of the acronym LEA *(1 mark)*
(f) What is a mnemonic? *(1 mark)*
(g) List any four logical operators used in assembly language *(1 mark)*

QUESTION TWO

(12 marks)

2. (a) What is an Adder? *(1 mark)*
(b) Given a 1 Bit full adder:
i. Construct the truth table for 1Bit Full Adder *(4 mark)*
ii. Simplify SOP for Sum *(1 mark)*

- iii. Simplify SOP for Carry out (1 mark)
- iv. Draw Karnaugh map for Sum (1 mark)
- v. Draw Karnaugh map for Carry out (1 mark)
- vi. Draw logic circuit for minimized expression (3 marks)

QUESTION THREE (12 marks)

- 3 (a) i. What is a Flip-Flop? (3 marks)
- ii. Construct the Truth-Table for Positive Edge –Triggered S-R Flip-Flops (4 marks)
- iii. Construct the Truth-Table for Negative Edge –Triggered S-R Flip-Flops (4 marks)
- (b) List three different types of edge-triggered flip-flops are generally used in digital logic circuits. (1 mark)

QUESTION FOUR (12 marks)

- (a) Distinguish between Moore State Machine and Mealy State Machine (8 marks)
- (b) State in tabular form the input and output of an Edge-Detector transitions between two symbols in the input sequence, say 0 and 1 using sequence of pairs for minimum of FIVE different number of possible pairs. (4 marks)

QUESTION FIVE (12 marks)

- (a) Differentiate between RAM and ROM (4 marks)
- (b) List and explain different Types of ROM (5 marks)
- (c) Explain different Types of DRAMS (3 marks)

QUESTION SIX (12 marks)

- (a). Construct the Truth-table for a 3-to-8 encoder with enable (5 marks)
- (b). List SIX important Flip-Flop Operating Characteristics (3 marks)
- (c). Explain any FOUR Flip-Flop Operating Characteristics (4 marks)