



NATIONAL OPEN UNIVERSITY OF NIGERIA
University Village, 91 Cadastral Zone, Nnamdi Azikwe Expressway, Jabi, Abuja
FACULTY OF SCIENCES
COMPUTER SCIENCE DEPARTMENT
2021 EXAMINATIONS

CIT 344 – Introduction To Computer Design


Credit: 3 units

TIME ALLOWED: 2½ Hours

INSTRUCTION: Answer Question 1 and any other FOUR (4) Questions

QUESTION ONE (22 marks)

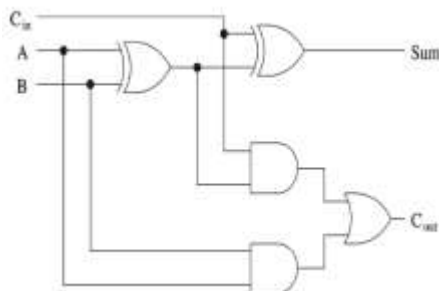- (a)
 - i. Convert the fraction decimal 600.88 to binary (2 mark)
 - ii. Convert fraction binary number 11101.11 to decimal equivalent (2 mark)
 - iii. Carry out the binary multiplication of 1110011 and 1100 (2 mark)
 - iv. Convert the binary number 1110011 to hexadecimal (1 mark)
- (b) Distinguish between BCD and Gray Code (2 marks)
- (c) Explain the steps required for the design of a Combinational Logic Circuit (3 marks)
- (d) Construct the truth table for the logic circuit given below: (3½ marks)



- (e) Simplify the expression $\overline{A} \overline{B} C + \overline{A} B \overline{C} + \overline{A} B C + A B C$ (1½ marks)
- (f) What is the function of a multiplexer? (1 mark)
- (g) What is a Priority Encoder? (2 marks)
- (h) Construct the truth table for NOR based S-R Latch (2 marks)

QUESTION TWO (12 marks)

- (a) Construct the truth table for Truth Table of a Gated D Latch (3½ marks)
- (b) List the three different types of edge-triggered flip-flops are generally used in digital logic circuits. (3 marks)

- (c) What are the features of 74HC74 flip=flop? (2 marks)
- (d) Convert 675_8 to base two (2 ½ mark)
- (e) What is the meaning of BCD? (1 mark)

QUESTION THREE (12 marks)

- (a) Draw the diagram for 11-Bit Serial Data converter (3 marks)
- (b) What is a sequencer? (2 marks)
- (c) Give the meaning of the acronym MIDI (1 mark)
- (d) What are the characteristics of MIDI sequencer? (4 marks)
- (e) What is a transducer? (2 marks)

QUESTION FOUR (12 marks)

- (a) Draw a diagram for Traffic Light Sequencer (3 marks)
- (b) Draw a diagram for 64-Cell Memory Array (4 marks)
- (c) Evaluate this expression $(P \wedge \neg Q) \vee \neg(P \vee Q)$ using Truth Table (5 marks)

QUESTION FIVE (12 marks)

- (a) Draw the Circuit Diagram of a Static Memory Cell based on a Flip-Flop (5 marks)
- (b) What are the characteristics of Static RAM (3 marks)
- (c) What is the drawback of DRAM? (1½ mark)
- (d) Convert the hexadecimal AF56C to binary (2½ marks)

QUESTION SIX (12 marks)

- (a) What is the meaning of acronym MOSFET (2 marks)
- (b) What is FLASH memory? (3 marks)
- (c) Give the characteristics of any three types of memory in tabular form (7 marks)