



NATIONAL OPEN UNIVERSITY OF NIGERIA
University Village, 91 Cadastral Zone, Nnamdi Azikwe Expressway, Jabi, Abuja
FACULTY OF SCIENCES
APRIL, 2019 EXAMINATIONS

COURSE CODE: CIT344

COURSE TITLE: Introduction to Computer Design

CREDIT: 3 Units

TIME ALLOWED: 2½ Hours

INSTRUCTION: Answer Question 1 and any other FOUR (4) Questions

- 1a) Briefly explain the Repeated Division-by-2 method. *(4 marks)*
- b) Convert 111010110101110010110 in binary to Octal *(2 marks)*
- c) State the advantages of assembly language over high level languages. *(4 marks)*
- d) Compare the ASCII code and the Extended ASCII code *(3 marks)*
- e) Briefly explain the term combinational logic circuit. *(2½ marks)*
- f) Complete the Logic Function Generator based on 3-Variable Logic Function Table below:
(2 marks)

Input			Output
A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- g) State the following the Sum and the Carry-out Boolean expressions for a Full-Adder.
(3 marks)

- h) List the three different types of edge-triggered flip-flops generally used in digital logic circuits. *(1½ marks)*

- 2a) Briefly explain how a combinational logic circuit can be analysed and designed.
(6 marks)

- b) What is a DeMUX? *(2 marks)*
- c) List two (2) forms of DeMUX. *(2 marks)*
- d) What is a Gray code? *(2 marks)*

- 3a) What do you understand by the term 'decoder'? *(2 marks)*

- b) Give the truth table and logic symbol of a 2-to-4 Decoder. (3 marks)
 - c) Distinguish between Jumps and Loops (2 marks)
 - d) List the five ways of modeling the behaviour of finite state machines (5 marks)
- 4a) Enumerate any four different forms of Call instructions. (4 marks)
- b) State the functions of the **far** call instruction (4 marks)
 - c) Briefly describe a sequencer, giving at least one example of a sequencer. (2 marks)
 - d) Write short notes on Read and Write Signals. (2 marks)
- 5a) State the functions of the **near** call instruction (3 marks)
- b) State the function of an edge-detector? How does it perform this function? (2 marks)
 - c) Describe the Displacement-only addressing mode (5 marks)
 - d) State four uses of Edge-Triggered J-K Flip-Flops. (2 marks)
- 6a) State the two basic operations performed on memories and the signals typically used to support them. (6 marks)
- b) State the two major functions of a register. (2 marks)
 - c) Outline four of the different forms of shift operations of a register. (4 marks)