



**NATIONAL OPEN UNIVERSITY OF NIGERIA**  
**University Village, Nnamdi Azikiwe Expressway, Plot 91, Cadastral Zone, Jabi, Abuja**  
**FACULTY OF SCIENCES**  
**DEPARTMENT OF PURE AND APPLIED SCIENCE**  
**JANUARY 2018 EXAMINATION QUESTIONS**

**COURSE CODE: PHY405**

**COURSE TITLE: Electronics III**

**COURSE UNIT: 3 units**

**Time: 3 hours**

**ANSWER QUESTIONS ONE AND ANY FOUR OTHER QUESTIONS**

- Q.1a. Distinguish between BCD and A5C11 code. (3 marks)
- b. State Boolean theorems. (4 marks)
- c. With the aid of the diagram, show the realisation of AND, OR and NOT gates from NAND gates. (5 marks)
- d. Differentiate between rise time and fall time (3 marks)
- ii. State the expression for duty cycle (3 marks)
- e. If the time div control is set to  $2\mu/\text{div}$  and the displayed signal covers 4 div on the Horizontal scale of the cathode ray tube (CRT) screen, determine the frequency of the Signal. (4 marks)
- Q.2a. (i) What does MSP mean? (3 marks)
- (ii) What are the fundamental rules guiding the use of MSP (3 marks)
- b. Find the MSP expression for:
- (i)  $y = A\bar{B}\bar{C} + AB\bar{C} + ABC$  (3 marks)
- (ii)  $y = (\bar{A} + \bar{B})\bar{C} + \bar{A}\bar{B}$  (3 marks)
- Q.3a. State the methods of obtaining the truth table from a Boolean Expression. (4 marks)
- b. Sketch and label the following:
- (i) Graphic summary of De Morgan's theorems. (3 marks)
- (ii) The symbol of (a) half adder (2.5 marks)
- (b) full adder (2.5 marks)
- Q.4a. Distinguish between RAM and ROM (5 marks)
- b. (i) what is register? (3 marks)
- (ii) Describe the functioning of shift register (5 marks)
- Q. 5 a. Briefly explain with examples signal generator. (4 marks)
- b. State the different wave shapes and sketch the waveforms. (5 marks)
- c. Write the expression for determining the maximum amplitude of the triangular out,  $V_{02}$  (3 marks)
- Q.6a. Explain briefly how voltage can be measured with an oscilloscope. (4 marks)
- b (i) State six major subsystems of oscilloscope
- (ii) What are the four major components of cathode ray tube (CRT) and state their functions.