

1. The Exclusive-OR of variables $A = 1$ and $B = 0$ equals _____

1

2. One of the option is an example of optical memory

CD-ROM

3. Which of the following is not an addressing scheme

Delayed Addressing

4. Sum of products form can be implemented using _____ gates.

NAND gates

5. AND gate is an electronic circuit that gives a high output (1) only if _____.

all its inputs are high.

6. The NAND and NOR gates are called _____

Universal Functions

7. Product of sums form can be implemented using _____

NOR gates

8. Direct memory access involves the following components EXCEPT

CPU

9. How many RAID levels are there?

6

10. The NAND gate is equal _____

an AND gate followed by a NOR gate

Whatsapp: 08089722160 or click here for TMA assistance

Practice E-exams & Chat with course mates on [noungeeks.net](https://www.noungeeks.net)

Join group: [T.me/NOUNSTUDENTSFORUM](https://t.me/NOUNSTUDENTSFORUM)
CLICK TO DOWNLOAD MORE TMA PQ

Whatsapp: 08089722160 or click here for TMA assistance

Practice E-exams & Chat with course mates on noungeeks.net