

1. Memory elements in clocked sequential circuits are called flip-flop
2. Design procedure of sequential circuit is based on 8 steps
3. When the output of a tri state shift register is disabled, the output level is placed in a float state and a high impedance state
4. Synchronous counters eliminate the delay problems encountered with asynchronous (ripple) counters because the input clock pulses are applied simultaneously to each stage
5. Which type of device may be used to interface a parallel data format with external equipments serial format?
UART
6. What is meant by parallel loading the register?
Loading data in all four flip-flops at the same time
7. In Moore models, output are function of only present state
8. A sequence of equally spaced timing pulses may be easily generated by which type of counter circuit?
shift register sequencer
9. Mod 6 and mod 12 counters are most commonly used in digital clocks
10. A comparison between ring and johnson counters indicates that ___
a johnson counter has an inverted feedback path

Whatsapp: 08089722160 or click here for TMA assistance

Practice E-exams & Chat with course mates on noungeeks.net