

NATIONAL OPEN UNIVERSITY OF NIGERIA
PLOT 91, CADASTRAL ZONE, NNAMDI AZIKIWE EXPRESSWAY, JABI - ABUJA
FACULTY OF SCIENCES

DEPARTMENT OF PHYSICS

2024 I EXAMINATION

COURSE CODE: PHY 405
COURSE TITLE: ELECTRONICS III
CREDIT UNIT: 3
TIME ALLOWED: (3 HRS)

INSTRUCTION: *Answer question 1 and any other THREE questions*

Question 1

- i. What are registers? 4marks
- ii. Identify the LSB and MSB in this number 10000010000111 2marks
- iii. Convert these binary numbers to hexadecimal 0011101101111110 and 111010010110 6marks
- iv. Prove $A + AB = A$ 4marks
- v. Sketch a waveform for this binary number 110001110 3marks
- vi. Design this expression $Y = AB + BC + AC$ using logic gate 6marks

Question 2

- i. List and draw the basic combinational logic gates with their truth tables 3marks
- ii. Sketch the circuit diagrams for basic logic gates using diodes and transistors 6marks
- iii. Deduce the MSP expression for the following expression i. $Y = (A + B)C + AB$ ii. $Y = AB + A(B + C) + B(B + C)$. 6marks

Question 3

- i. Generate the truth tables and symbols for i. XOR ii. XNOR and NAND gates 6marks
- ii. Sketch the circuit for the following systems i. Half adder ii. Full adder 5marks
- iii. Draw a digital circuit for a 4-bit binary adder 4marks

Question 4

- i. List the major components of a general-purpose CRT 4marks
- ii. Draw the block diagram of a dual trace oscilloscope 5marks
- iii. Define the following (i) Rise Time (ii) Fall Time (iii) Duty cycle 6marks

Question 5

- i. What is computer memory? 3marks
- ii. Define and give 2 examples of active and passive components 6marks
- iii. Define and give examples of Volatile and Non-volatile memory 6marks

Question 6

- i. Design a buffered register? 3marks
- ii. Obtain the truth table for the following Boolean expression $Y = A + AB + CA$ 6marks
- iii. In tabular form distinguish between sequential and combinational circuits with examples 6marks